



TASK 2 VHDL

Amit Nagar- Halevy and Tal Kapelnik
204210306 204117089




Contents


Blocks diagram:	2
Logic usage:	3
Maximal operating clock:	4
Longest path:	4
Shortest Path:	5
Single-Tap HardWare Test:	6
Add test:	6
Mac test:	7
Shifter test:	7
Conclutions:	Error! Bookmark not defined.

Blocks diagram:

Top:

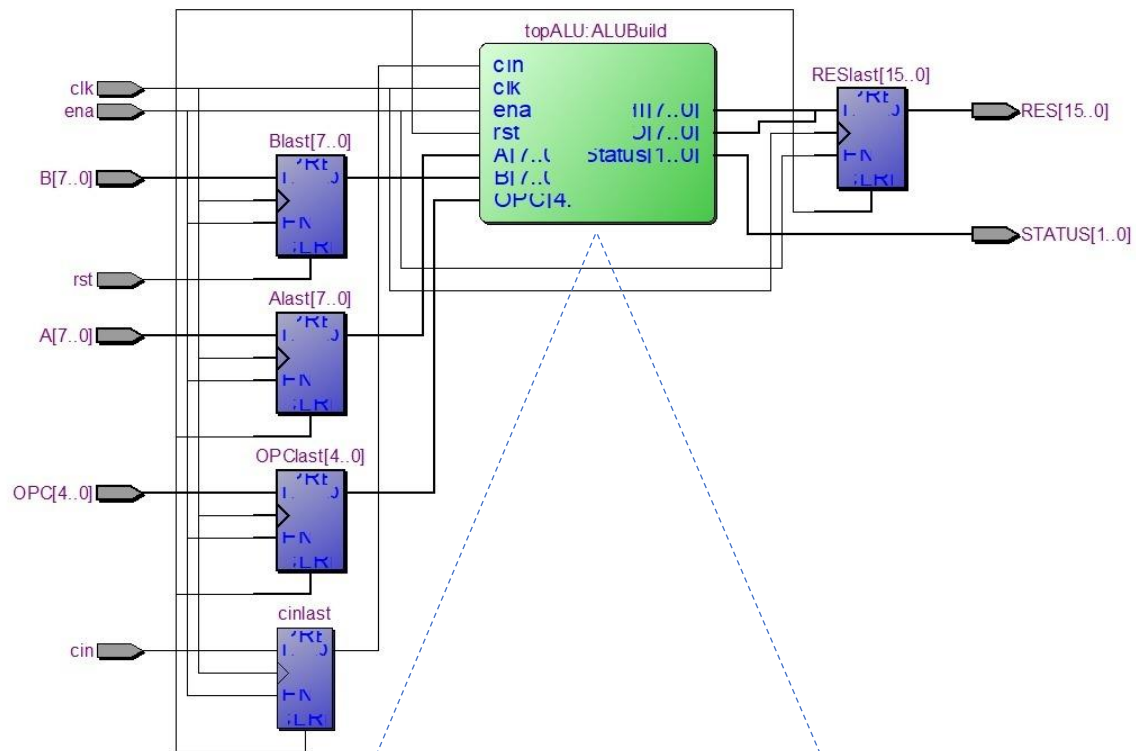

TopALU-subentity:

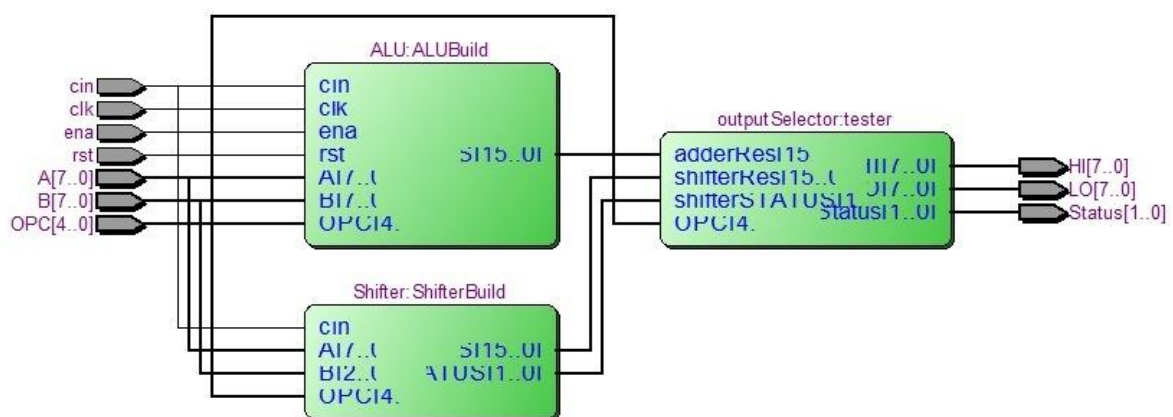

Logic usage:

Top:

Analysis & Synthesis Summary	
Analysis & Synthesis Status	Successful - Thu Jun 04 13:07:03 2020
Quartus II 64-Bit Version	12.1 Build 177 11/07/2012 SJ Web Edition
Revision Name	top
Top-level Entity Name	top
Family	Cyclone II
Total logic elements	270
Total combinational functions	248
Dedicated logic registers	72
Total registers	72
Total pins	43
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	1
Total PLLs	0

We can see that we used 1 Multiplier, 72 registered and total of 270 logic elements.

TopALU-subentity:

Analysis & Synthesis Resource Usage Summary		
	Resource	Usage
1	Estimated Total logic elements	250
2		
3	Total combinational functions	250
4	Logic element usage by number of LUT inputs	
1	-- 4 input functions	122
2	-- 3 input functions	101
3	-- <=2 input functions	27
5		
6	Logic elements by mode	
1	-- normal mode	228
2	-- arithmetic mode	22
7		
8	Total registers	32
1	-- Dedicated logic registers	32
2	-- I/O registers	0
9		
10	I/O pins	43
11	Embedded Multiplier 9-bit elements	1
12	Maximum fan-out	42
13	Total fan-out	975
14	Average fan-out	2.98

We can see that we used $72 - 32 = 40$ registered just for the top level, for saving all the data.


Maximal operating clock:

we have found that the maximum frequency is 121.39Mhz

Slow Model Fmax Summary				
	Fmax	Restricted Fmax	Clock Name	Note
1	121.39 MHz	121.39 MHz	clk	


So the Maximal operating clock is $\frac{1}{121.39\text{Mhz}} = 8.3\text{ns}$

Longest path:

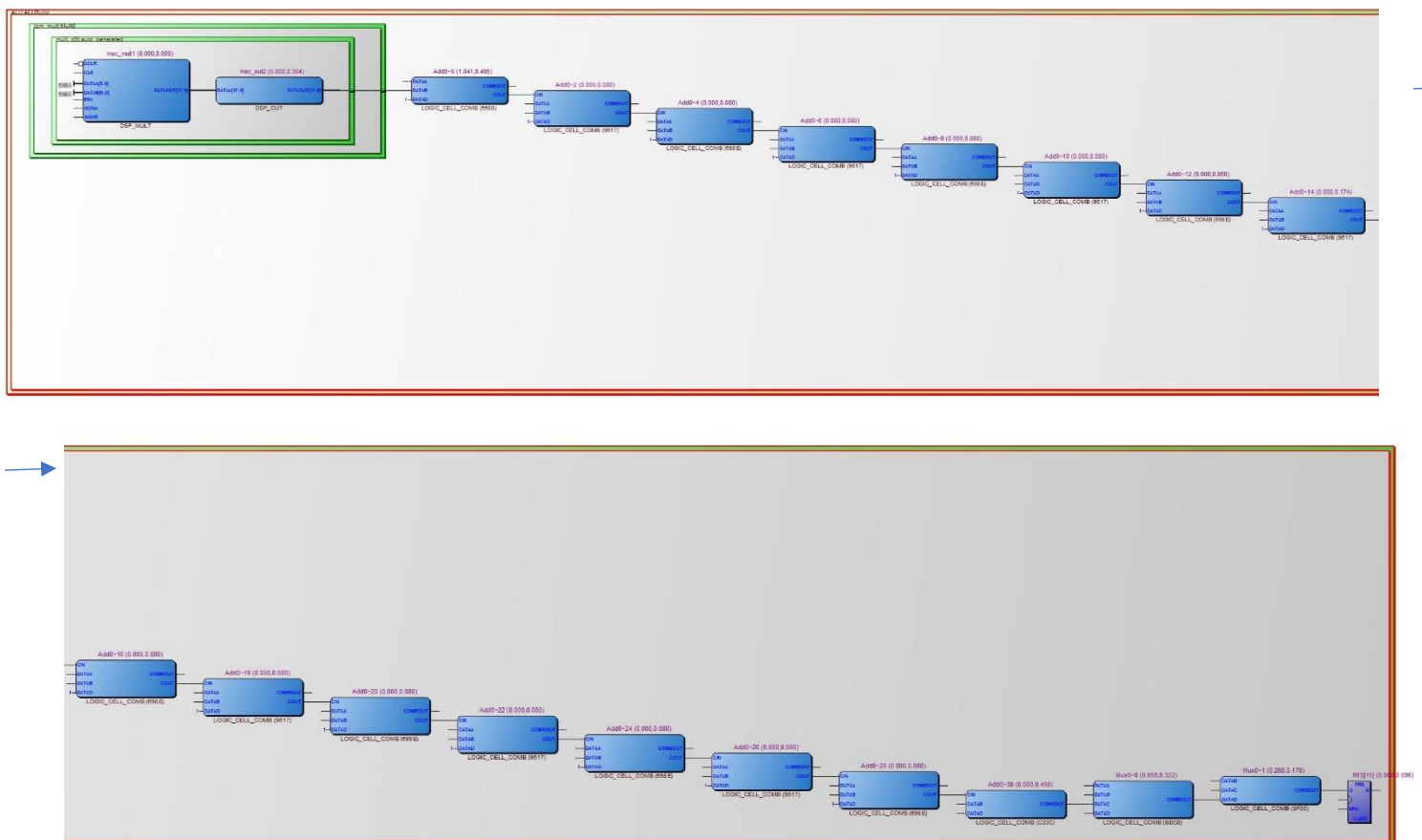

We can see that the longest path goes through the Multiplexer, it makes sense because its the most complex calculation we can do in this task.

Shortest Path:

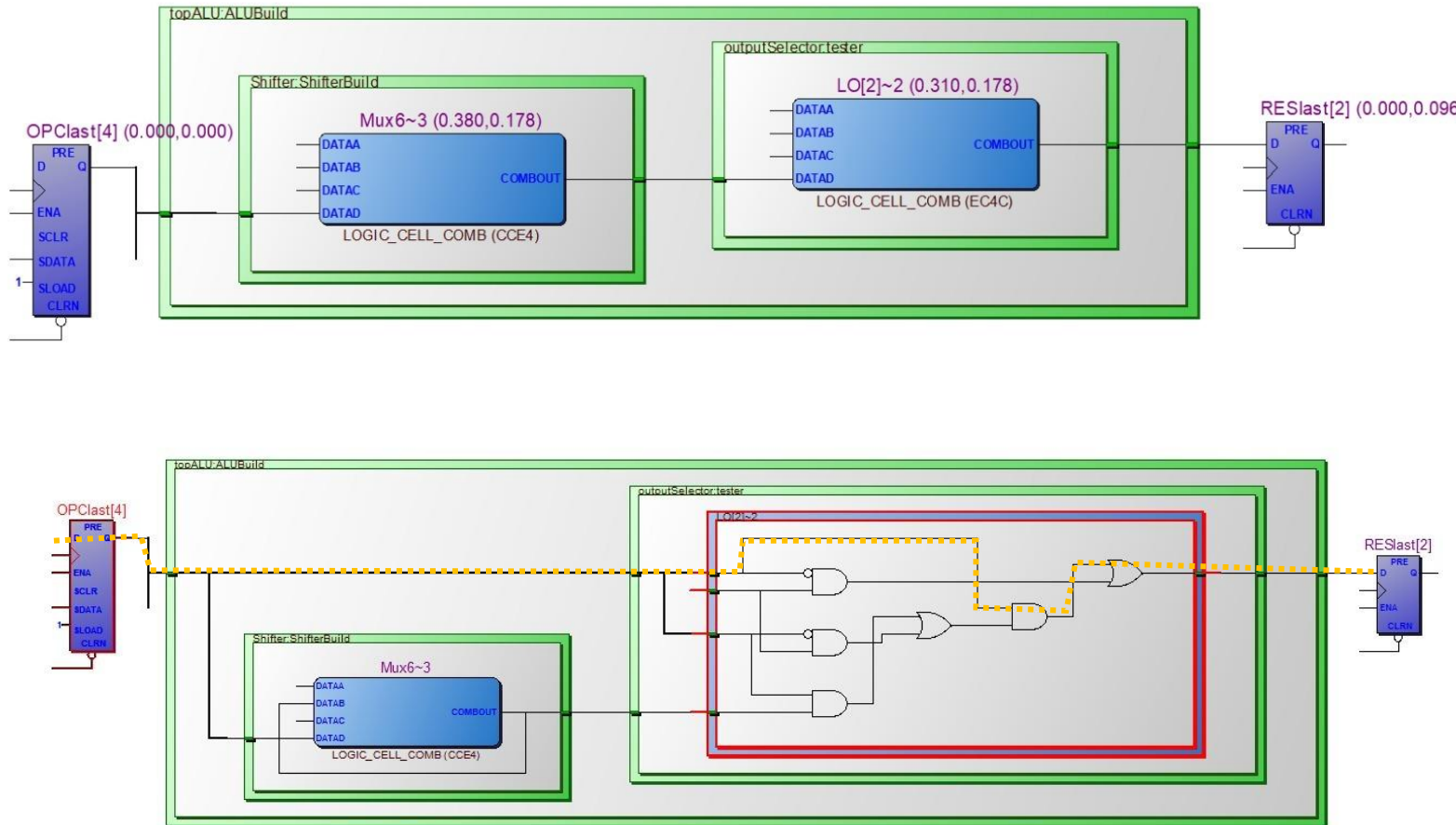

We only use OPC[4] for the output selector.

We don't use it for the Shifter or ALU entities.

so it makes sense it is the shortest path from start to finish.

Hardware Test Case:


For the hardware test, we've disabled all the clk's from our code, we have changed the input from A,B and OPC to REGISTER, and KEY0-2 decided where the REGISTER goes (A B or OPC).

We've also added a process for the case where Key3 is pressed.

Single-Tap HardWare Test:


Add test:

 we added $01h + 01h = 02h$, and then we changed A to $05h$ so the result was $06h$.




Mac test:

Button Key2 pushed -> B became 05(h)

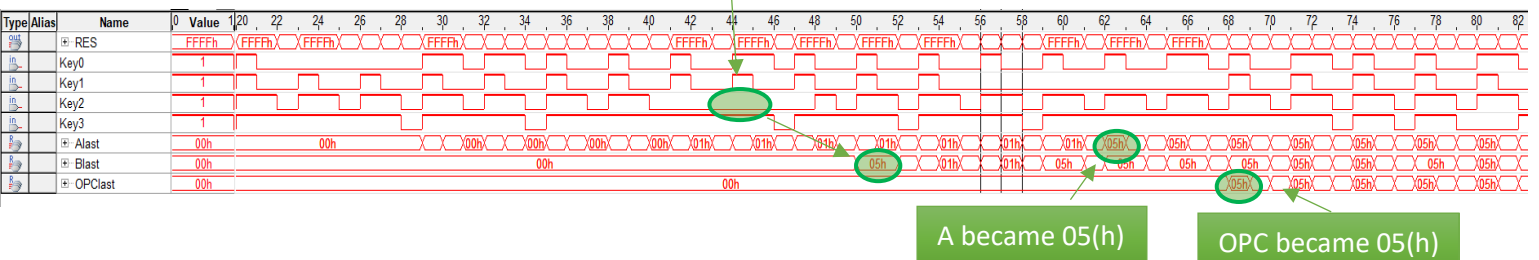

Result became 16(h)

 

Shifter test:

we've put in $A=EF(h)$ and in $B=01(h)$ and the $OPC=01101$, so we got in the result $=DF(h)$, so we've got one rotation left through carry as expected.

Result = DF(h)

